

# Objective

In this lab, students were introduced to latches and flip-flops. These sequential logic circuits will be described in first structural Verilog and then behavioral Verilog. Synchronous sequential circuits will also be introduced towards the end of the lab. Delays will also be added to logic gates for the first time while implementing a clock signal. Finally, students will design one block of code that will include both flip-flops and combinational logic (full adder) to simulate synchronous logic.

## Design

### Experiment 1

To start off the experiment, a structural Verilog SR-Latch was designed. Two nanoseconds delays were added to the gates. After that, the delay was increased to four nanoseconds. Below is the code for which the four nanosecond delay was designed for. For a two nanosecond design, instead of #4, there was #2.

Code Block 1: SR-Latch

```
1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Create Date: 14:49:20 10/24/2016
4  // Module Name: sr_latch
5  // Author Name: Joseph Martinsen
6  //
7  ///////////////////////////////////////////////////////////////////
8
9  module sr_latch (Q, notQ, En, S, R);
10     // All ports should be wires
11     output wire Q, notQ;
12     input wire En, S, R;
13
14     // Intermediate nets
```

```

15  wire nandSEN, nandREN;
16
17  // 4ns delay
18  nand #4 nand0(Q, nandSEN, notQ);
19  // finish things up here...
20  nand #4 nand1(notQ, nandREN, Q);
21  nand #4 nand2(nandSEN, S, En);
22  nand #4 nand3(nandREN, R, En);
23 endmodule // sr_latch

```

Next, a structural D-Latch was designed. The design took into consideration that NOT and NAND gates had a two nanosecond delay each. Below is the design for the structural D-Latch.

Code Block 2: D-Latch

```

1  'timescale 1ns / 1ps
2  ////////////////////////////////////
3  // Create Date: 15:27:40 10/24/2016
4  // Module Name: d_latch
5  // Author Name: Joseph Martinsen
6  //
7  ////////////////////////////////////
8
9  module d_latch(Q, notQ, En, D);
10  // Declare Wires
11  output wire Q;
12  output wire notQ;
13  input wire En;
14  input wire D;
15
16  // Declare Intermediate Wires
17  wire Dnot;

```

```

18  wire nandDnotEN;
19  wire Dn1;
20
21  // Structural Logic for D-Latch
22      not #2 (Dnot, D);
23      nand #2 nand0(nandDEN, D, En); //2ns gate delay
24      nand #2 nand1(Q, nandDEN, notQ);
25      nand #2 nand2 (nandDnotEN, Dnot, En);
26      nand #2 nand3 (notQ, Q, nandDnotEN);
27 endmodule // d_latch

```

The next part of **Experiment 1** consisted of designing a D flip-flop in structural Verilog. The design instantiated only two inverter gates and two D-latch modules that were designed earlier in this lab. The design for the structural D flip-flop.

Code Block 3: D FLip-FLop

```

1  'timescale 1ns / 1ps
2  ////////////////////////////////////
3  // Create Date: 15:44:29 10/24/2016
4  // Module Name: d_flip_flop
5  // Author Name: Joseph Martinsen
6  //
7  ////////////////////////////////////
8  module d_flip_flop (Q, notQ, Clk, D);
9      output wire Q, notQ;
10     input wire Clk, D;
11
12     // Internal nets
13     wire notClk, notNotClk;
14     wire Q_m; // Output of master latch
15     // notQ_m will be wired to the d_latch but then left
16     // unconnected from there

```

```

17  wire notQ_m;
18
19  // Structural level wiring
20  // Instantiate and wire up the not gates here...
21  not #2 not0(notClk, Clk);
22  not #2 not1(notNotClk, notClk);
23
24  // Instantiate and wire up the d latches based
25  // on schematic in lab
26  d_latch dlMaster(Q_m, notQ_m, notClk, D);
27  d_latch dlSlave(Q, notQ, notNotClk, Q_m);
28 endmodule // d_flip_flop

```

Next, a behavioral version of the D-latch and D flip-flop was copied and edited from the lab manual. The following designs are below. *Compare the waveforms you captured from the behavioral Verilog to those captured from the structural Verilog. Are they different? If so, how?*

#### Code Block 4: D-Latch Behavioral

```

1  'timescale 1ns / 1ps
2  ////////////////////////////////////
3  // Create Date: 16:00:39 10/24/2016
4  // Module Name: d_latch_behavioral
5  // Author Name: Joseph Martinsen
6  //
7  ////////////////////////////////////
8  module d_latch_behavioral(
9      // Declare Input/Output Wires
10     output reg Q,
11     output wire notQ,
12     input wire D, En
13 );

```

```

14
15      // Logic for D-Latch
16      always@(En or D)
17          if(En)
18              Q = D;
19          else
20              Q = Q;
21      // Catch All
22      assign notQ = ~Q;
23 endmodule

```

Code Block 5: D Flip-Flop Behavioral

```

1  'timescale 1ns / 1ps
2  ////////////////////////////////////
3  // Create Date: 16:06:56 10/24/2016
4  // Module Name: d_flip_flop_behavioral
5  // Author Name: Joseph Martinsen
6  //
7  ////////////////////////////////////
8  module d_flip_flop_behavioral(
9      // Declare wires
10     output reg Q,
11     output wire notQ,
12     input wire D,
13     input wire Clk
14 );
15
16     // Logic for Positive Edge of Clock
17     always@(posedge Clk)
18         Q <= D;
19

```

```

20      // Catch all Case
21      assign notQ = ~Q;
22 endmodule

```

## Experiment 2

To start off **Experiment 2**, the full adder designed in **Lab 6** was modified. Gate delays were added such that 3-input AND, OR, and XOR gates have a delay of six nanoseconds, while 2-input AND, OR, and XOR gates have a delay of four nanoseconds. Finally, NOT, NAND, and NOR gates were changed in order to have a delay of two nanoseconds.

Code Block 6: Full Adder Edited

```

1  'timescale 1ns / 1ps
2  'default_nettype none
3  //////////////////////////////////////
4  // Create Date: 16:06:23 10/10/2016
5  // Module Name: full_adder
6  // Author Name: Joseph Martinsen
7  //
8  //////////////////////////////////////
9  module full_adder(S, Cout, A, B, Cin );
10     // Declare input and output ports
11     input wire A, B, Cin;
12     output wire S, Cout;
13
14     // Declare wires
15     wire andBCin, andACin, andAB; // add more
16
17     // Use dataflow to create gatelevel commands
18     assign #6 S = A ^ B ^ Cin; // ^ is XOR
19     assign #4 andAB = A & B;
20     assign #4 andBCin = B & Cin;

```

```

21         assign #4 andACin = A & Cin;
22         assign #6 Cout = andAB | andBCin | andACin;
23     endmodule

```

The edited full adder was then used to create a simple 2-Bit Adder. The design is below.

Code Block 7: 2-Bit Adder

```

1  'timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Create Date: 16:13:10 10/24/2016
4  // Module Name: adder_2bit
5  // Author Name: Joseph Martinsen
6  //
7  ///////////////////////////////////////////////////////////////////
8  module adder_2bit(Carry, Sum, A, B);
9      // Initialize Wires
10     output wire [1:0] Sum;
11     output wire Carry;
12     input wire [1:0] A;
13     input wire [1:0] B;
14     wire Cout;
15
16     // Call 2 Full adders to make it 2-Bit
17     full_adder fa0(Sum[0], Cout, A[0], B[0], 0);
18     full_adder fa1(Sum[1], Carry, A[1], B[1], Cout );
19
20 endmodule

```

The 2-Bit adder test bench was incomplete in order to check the soundness of the newly designed two-bit adder. After adding a test case for every output, the 2-Bit adder was then tested. The modified test bench is below. *Use the simulation waveform to*

determine the worst case propagation delay through the ripple- carry adder. 20ns

#### Code Block 8: 2-Bit Adder Test Bench

```
1 'timescale 1ns / 1ps
2
3 module add_2bit_tb;
4
5 /* Input nets */
6 reg [1:0] A; //these are regs because they are modified in
7 reg [1:0] B; //a behavioral block
8
9 /* Output nets */
10 wire [1:0] Sum; //these are wires because they will be driven
11 wire Carry; //by the inantiated module
12
13 /* Instantiate the Unit Under Test (UUT) */
14 adder_2bit uut ( //this is a different way
15 .A(A),          //to instantiate a module.
16 .B(B),          //the nice thing about this style
17 .Sum(Sum),      //is that the order does not matter!
18 .Carry(Carry) //notice the ports are in a different order!
19 );
20
21
22 /*-this is a behavioral block which is executed only once! *
23 *-the statements within this behavioral block are executed *
24 *-sequentially because we are using blocking statements *
25 *-an '=' sign within a behavioral construct is considered a*
26 * blocking statement. We will talk more about this later...*/
27 initial
28     begin
```



```

29
30  /* Initialize inputs*/
31  A = 0;
32  B = 0;
33
34  #25; //just delay 25 ns
35  {A,B} = 4'b0000; //stimulate the inputs
36  #25; //wait a bit for the result to propagate
37  //here is where we could put a check to see if the results
38  //are as expected!
39  if({Carry, Sum} != 3'b000)
40      $display("Ah_crap..._something_went_wrong_here...");
41      else
42          $display("Hey!_The_UUT_passed");
43  //let's do it again with a different input...
44  {A,B} = 4'b0001; //stimulate the inputs
45  #25; //wait a bit for the result to propagate
46  //check output
47  if({Carry, Sum} != 3'b001)
48      $display("You_are_garbage!");
49      else
50          $display("Test_vector_passed!!!");
51  //okay this is fun... you try it now...
52
53  //let's do it again with a different input...
54  {A,B} = 4'b0010; //stimulate the inputs
55  #25; //wait a bit for the result to propagate
56  //check output
57  if({Carry, Sum} != 3'b010)
58      $display("You_are_garbage!");
59      else

```

```

60         $display("Test_vector_passed!!!");
61
62         //let's do it again with a different input...
63         {A,B} = 4'b0011; //stimulate the inputs
64         #25; //wait a bit for the result to propagate
65         //check output
66         if({Carry, Sum} != 3'b011)
67             $display("You_are_garbage!");
68         else
69             $display("Test_vector_passed!!!");
70
71         //let's do it again with a different input...
72         {A,B} = 4'b0100; //stimulate the inputs
73         #25; //wait a bit for the result to propagate
74         //check output
75         if({Carry, Sum} != 3'b001)
76             $display("You_are_garbage!");
77         else
78             $display("Test_vector_passed!!!");
79
80         //let's do it again with a different input...
81         {A,B} = 4'b0101; //stimulate the inputs
82         #25; //wait a bit for the result to propagate
83         //check output
84         if({Carry, Sum} != 3'b010)
85             $display("You_are_garbage!");
86         else
87             $display("Test_vector_passed!!!");
88
89         //let's do it again with a different input...
90         {A,B} = 4'b0110; //stimulate the inputs

```

```

91      #25; //wait a bit for the result to propagate
92      //check output
93      if({Carry , Sum} != 3'b011)
94          $display("You_are_garbage!");
95          else
96              $display("Test_vector_passed!!!");
97
98          //let's do it again with a different input...
99      {A,B} = 4'b0111; //stimulate the inputs
100     #25; //wait a bit for the result to propagate
101     //check output
102     if({Carry , Sum} != 3'b100)
103         $display("You_are_garbage!");
104         else
105             $display("Test_vector_passed!!!");
106
107         //let's do it again with a different input...
108     {A,B} = 4'b1000; //stimulate the inputs
109     #25; //wait a bit for the result to propagate
110     //check output
111     if({Carry , Sum} != 3'b010)
112         $display("You_are_garbage!");
113         else
114             $display("Test_vector_passed!!!");
115
116         //let's do it again with a different input...
117     {A,B} = 4'b1001; //stimulate the inputs
118     #25; //wait a bit for the result to propagate
119     //check output
120     if({Carry , Sum} != 3'b011)
121         $display("You_are_garbage!");

```

```

122         else
123             $display("Test_vector_passed!!!");
124
125         //let's do it again with a different input...
126         {A,B} = 4'b1010; //stimulate the inputs
127         #25; //wait a bit for the result to propagate
128         //check output
129         if({Carry, Sum} != 3'b100)
130             $display("You_are_garbage!");
131         else
132             $display("Test_vector_passed!!!");
133
134         //let's do it again with a different input...
135         {A,B} = 4'b1011; //stimulate the inputs
136         #25; //wait a bit for the result to propagate
137         //check output
138         if({Carry, Sum} != 3'b101)
139             $display("You_are_garbage!");
140         else
141             $display("Test_vector_passed!!!");
142
143         //let's do it again with a different input...
144         {A,B} = 4'b1100; //stimulate the inputs
145         #25; //wait a bit for the result to propagate
146         //check output
147         if({Carry, Sum} != 3'b011)
148             $display("You_are_garbage!");
149         else
150             $display("Test_vector_passed!!!");
151
152         //let's do it again with a different input...

```

```

153 {A,B} = 4'b1101; //stimulate the inputs
154 #25; //wait a bit for the result to propagate
155 //check output
156 if({Carry, Sum} != 3'b100)
157     $display("You_are_garbage!");
158     else
159         $display("Test_vector_passed!!!");
160
161     //let's do it again with a different input...
162 {A,B} = 4'b1110; //stimulate the inputs
163 #25; //wait a bit for the result to propagate
164 //check output
165 if({Carry, Sum} != 3'b101)
166     $display("You_are_garbage!");
167     else
168         $display("Test_vector_passed!!!");
169
170     //let's do it again with a different input...
171 {A,B} = 4'b1111; //stimulate the inputs
172 #25; //wait a bit for the result to propagate
173 //check output
174 if({Carry, Sum} != 3'b110)
175     $display("You_are_garbage!");
176     else
177         $display("Test_vector_passed!!!");
178
179 $stop;
180 end
181
182 endmodule

```

In the final part of the lab, Verilog code was created to complete the synchronous aspect of the design. The flip-flops were assumed to be ideal thus it will not contribute to any time delay.

Code Block 9: Adder Synchronous

```

1  'timescale 1ns / 1ps
2  //////////////////////////////////////
3  // Create Date: 16:53:17 10/24/2016
4  // Module Name: adder_synchronous
5  // Author Name: Joseph Martinsen
6  //
7  //////////////////////////////////////
8  module adder_synchronous(Carry_reg , Sum_reg , Clk , A, B);
9      // Declare Wires
10     output reg Carry_reg;
11     output reg [1:0] Sum_reg;
12     input wire Clk;
13     input wire [1:0] A,B;
14     reg [1:0] A_reg , B_reg;
15     wire Carry;
16     wire [1:0] Sum;
17
18     // Instantiate 2-Bit Adder
19     adder_2bit a2b0(Carry , Sum, A_reg , B_reg);
20
21     // Logice for A and B
22     always@(posedge Clk)
23         begin
24             A_reg <= A;
25             B_reg <= B;
26         end

```

```

27
28      // Logice for Sum and Carry
29      always@(posedge Clk)
30          begin
31              Carry_reg <= Carry;
32              Sum_reg <= Sum;
33          end
34 endmodule

```

In the end, 'define CLOCK PERIOD in the test bench code was changed to 18, 19, and finally 20.

## Results

### Experiment 1

The first test was for the SR-Latch that had a two second delay for each gate.

```

-----
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
    SR-latch Reset Test passed
    SR-latch Hold 0 Test passed
    SR-latch Set Test passed
    SR-latch Hold 1 Test passed
SR-latch Reset from Set Test passed
SR-latch Enable Hold Test 1 passed
SR-latch Enable Hold Test 2 passed
SR-latch Enable Hold Test 3 passed
SR-latch Enable Hold Test 4 passed
All tests passed
Stopped at time : 100 ns : in File "/home/ugrads/j/josephmart/prelab/sr\_latch\_tb.v" Line 72

```

Figure 1: *SR Latch Test Results*

 


Figure 2: *SR Latch Graph*

The next test was again for the SR-Latch but this time, the gates had a four second delay instead of two. The test results are below.

```

-----
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
    SR-latch Reset Test failed: X should be 1
    SR-latch Hold 0 Test passed
    SR-latch Set Test failed: 3 should be 2
    SR-latch Hold 1 Test passed
    SR-latch Reset from Set Test failed: 3 should be 1
    SR-latch Enable Hold Test 1 passed
    SR-latch Enable Hold Test 2 passed
    SR-latch Enable Hold Test 3 passed
    SR-latch Enable Hold Test 4 passed
Some tests failed
Stopped at time : 100 ns : in File "/home/ugrads/j/josephmart/prelab/sr\_latch\_tb.v" Line 72

```

Figure 3: *SR Latch2 Test Results*



 


Figure 4: *SR Latch2 Graph*

The test for the four nanosecond delay failed the first four reset , hold, and set tests. For instances where the four delay was in line with the two delay, the test passed

Next, the D-Latch was tested against the provided test bench. The operation matched the given table in the lab. The test results are below.

```
-----
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
    D-latch Enable Test 1 passed
    D-latch Enable Test 2 passed
    D-latch Hold Test 1 passed
    D-latch Hold Test 2 passed
    D-latch Hold Test 3 passed
    D-latch Hold Test 4 passed
All tests passed
Stopped at time : 70 ns : in File "/home/ugrads/j/josephmart/prelab/d\_latch\_tb.v" Line 63
|
```

Figure 5: *D-Latch Test Results*

 


Figure 6: *D-Latch Graph*

The D flip-flop was then tested against the appropriate test bench with internal nets in the waveform.

```
-----
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
  D flip-flop Store 0 Test passed
  D flip-flop Hold 0 Test passed
    D flip-flop Store 1 passed
    D flip-flop Hold 1 Test passed
  flip-flop Store 0 Test Again... passed
All tests passed
Stopped at time : 211 ns : in File "/home/ugrads/j/josephmart/prelab/d\_flip\_flop\_tb.v" Line 71
```

Figure 7: *D Flip-Flop Tests*



Figure 8: *D Flip-Flop Graph*

The internal nets behaved as expected.

In the final part of **Experiment 1**, the behavioral D-Latch and D flip-flop was tested against their appropriate test benches.

```
-----
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
  D-latch Enable Test 1 passed
  D-latch Enable Test 2 passed
  D-latch Hold Test 1 passed
  D-latch Hold Test 2 passed
  D-latch Hold Test 3 passed
  D-latch Hold Test 4 passed
All tests passed
Stopped at time : 70 ns : in File "/home/ugrads/j/josephmart/ecen248/lab08/d\_latch\_behavioral\_tb.v" Line 63
```

Figure 9: *D Latch Behavioral Test Results*

 


Figure 10: *D Latch Behavioral Graph*

-----  
 This is a Full version of ISim.  
 Time resolution is 1 ps  
 Simulator is doing circuit initialization process.  
 Finished circuit initialization process.  
     D flip-flop Store 0 Test passed  
     D flip-flop Hold 0 Test passed  
     D flip-flop Store 1 passed  
     D flip-flop Hold 1 Test passed  
 flip-flop Store 0 Test Again... passed  
 All tests passed  
 Stopped at time : 211 ns : in [File "/home/ugrads/j/josephmart/ecen248/lab08/d\\_flip\\_flop\\_behavioral\\_tb.v" Line 71](#)

Figure 11: *D Flip Flop Behavioral Test Results*







Figure 16: *Async 40 Graph*

This is a Full version of ISim.  
 WARNING: For instance a2b0/fa0/, width 1 of formal port Cin is not equal to width 32 of actual constant.  
 Time resolution is 1 ps  
 Simulator is doing circuit initialization process.  
 Finished circuit initialization process.  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test failed: 07 should be 03  
 Synchronous Adder Test failed: 00 should be 04  
 Synchronous Adder Test failed: 06 should be 02  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test passed  
 Synchronous Adder Test failed: 00 should be 04  
 Synchronous Adder Test passed  
 Some tests failed  
 Stopped at time : 297 ns(1) : in [File "/home/ugrads/josephmart/ecen248/lab08/adder\\_synchronous\\_tb.v" Line 78](#)

Figure 17: *Async 18 Tests*

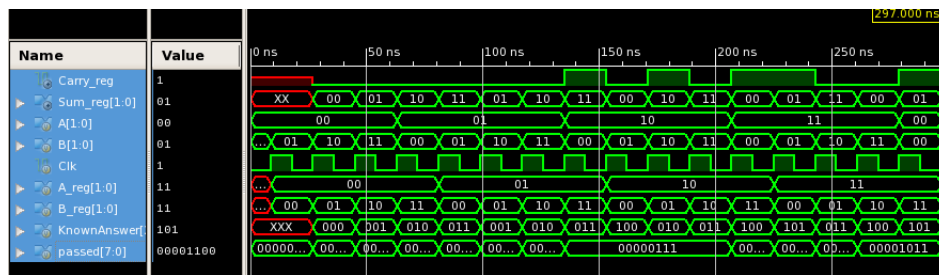


Figure 18: *Asyc 18 Graph*

This is a Full version of ISim.

**WARNING:** For instance a2b0/fa0/, width 1 of formal port Cin is not equal to width 32 of actual constant.

Time resolution is 1 ps

Simulator is doing circuit initialization process.

Finished circuit initialization process.

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

Synchronous Adder Test passed

All tests passed

Stopped at time : 330 ns(1) : in [File "/home/ugrads/j/josephmart/ecen248/lab08/adder\\_synchronous\\_tb.v" Line 78](#)

Figure 19: *Async 20 Tests*





Figure 20: *Async 20 Graph*

The test passed for 40 and 20 and failed for 18 and 19. Thus the shorest '*defineCLOCKPERIOD* = 20ns

## Conclution

In conclution, this lab exposed me to test bench code by allowing me to create my own for the first time. Also, this lab introduced me to three different type of latches, SR latch, D latch, and D flip-flop latch.

## Questions

1. Include the source code with comments for all modules you simulated. You do not have to include test bench code that that was provided; however, you must supply the test bench code that you wrote! Code without comments will not be accepted.

*In the report.*

2. **Include screenshots of all waveforms captured during simulation in addition to the test bench console output for each test bench simulation.**

*In the report.*

3. **Answer all questions throughout the lab manual.**

*In the report.*

4. **Compare the behavioral description of the synchronous adder found in the test bench code with the combination of structural and dataflow Verilog you used in the lab assignment. What are the advantages and disadvantages of each? Which do you prefer and why?**

The advantage of utilizing a behavioral description is that it is very simple and to the point because it uses one statement that then decides what kind of output it is going to be. In structural and dataflow Verilog it is precise, but not all that concise. Efficiency is lost because it must look for each specific output rather than just paying attention to the output behavior as a whole. I prefer behavioral Verilog because it seems like it is a whole lot more efficient.

5. **Based on the clock period you measured for your synchronous adder, what would be the theoretical maximum clock rate? What would be the effect of increasing the width of the adder on the clock rate? How might you improve the clock rate of the design?**

The smallest 'define CLOCK PERIOD that the circuit could of been reduced to and still function was 20 ns which works at a 50MHz clock rate. Increasing the width of the adder would cause the clock rate to drop because it has to work with more inputs. This would result in a greater time delay which would result in a drop in clock rate. Improving the clock rate of the design would be done by decreasing the time delay in the circuit by simplifying the circuit have to use less or by using gates that have a smaller gate delay.

## Student Feedback

1. **What did you like most about the lab assignment and why? What did you like least about it and why?**

I enjoyed learning about test bench workings. I also liked practicing more with Verilog.

2. **Were there any section of the lab manual that were unclear? If so, what was unclear? Do you have any suggestions for improving the clarity?**

This lab was very straight forward and provided more guidance than most of the previous labs.

3. **What suggestions do you have to improve the overall lab assignment?**

Synthesising the designs onto the Spartan board would have been cool.