

Prelab Questions

1. With dataflow Verilog, describe the Generate/Propagate Unit, the Carry-Lookahead Unit, and the Summation Unit in Figure 1 as separate modules. Do not include delays in your modules. We will add them later in the lab experiments.

Code Block 1: Generate Propagate Unit

```
1 // This module describes the Carry Generate/Propagate
2 // Unit for a 4-bit carry-lookahead addition
3 module generate_propagate_unit(G, P, X, Y);
4
5     // Ports are wires as we will use dataflow
6     output wire [3:0] G, P;
7     input wire [3:0] X, Y;
8
9     assign G[0] = X[0] & Y[0];
10    assign G[1] = X[1] & Y[1];
11    assign G[2] = X[2] & Y[2];
12    assign G[3] = X[3] & Y[3];
13
14    assign P[0] = X[0] ^ Y[0];
15    assign P[1] = X[1] ^ Y[1];
16    assign P[2] = X[2] ^ Y[2];
17    assign P[3] = X[3] ^ Y[3];
18
19 endmodule // generate_propagate_unit
```

Code Block 2: Carry Lookahead Unit

```
1 // This module describes the 4-bit carry-lookahead Unit
2 // for a carry-lookahead adder
3 module carry_lookahead_unit (C, G, P, C0);
```

```

4    // Ports are wires because we will use dataflow
5    output wire [4:1] C; // C4, C3, C2, C1
6    input wire [3:0] G, P; // Generates and propagates
7    input wire C0; // input carry
8
9    assign C[1] = G[0] || (P[0] & C0);
10   assign C[2] = G[1] || (P[1] & G[0]) || (P[1] & P[0] & C[0]);
11   assign C[3] = G[2] || (P[2] & G[1]) || (P[2] & P[1] & G[0])
12       || (P[2] & P[1] & P[0] & C[0]);
13   assign C[4] = G[3] || (P[3] & G[2]) || (P[3] & P[2] & G[1])
14       || (P[3] & P[2] & P[1] & G[0]) || (P[3] & P[2] & P[1] &
15       P[0] & C[0]);
16
17 endmodule // carry_lookahead_unit

```

Code Block 3: Summation Unit

```

1    // This module describes the 4-bit summation Unit
2    // for a carry-lookahead adder
3
4    module summation_unit (S, P, C);
5
6    // Ports are wires because we will use dataflow
7    output wire [3:0] S; // sum vector
8    input wire [3:0] P, C;
9
10   assign S[0] = P[1] ^ C[1];
11   assign S[2] = P[2] ^ C[2];
12   assign S[3] = P[3] ^ C[3];
13   assign S[4] = P[4] ^ C[4];
14
15 endmodule // summation_unit

```

-
2. Now, use structural Verilog along with the modules you have just created to wire up a 4-bit Carry-Lookahead adder.

Code Block 4: Carry Lookahead 4-Bit

```
1 // This is the top-level module for a 4-bit
2 // carry-lookahead adder
3
4 module carry-lookahead_4bit (Cout, S, X, Y, Cin);
5
6     // Ports are wires because we are using structural
7     output wire Cout; // C4 for a 4-bit adder
8     output wire [3:0] S; // final 4-bit sum vector
9     input wire [3:0] X, Y; // the 4-bit addends
10    input wire Cin; // input carry
11
12    // Intermediate wires
13    wire [3:0] G, P;
14    wire [4:1] C;
15
16    // generate_propagate_unit(G, P, X, Y);
17    generate_propagate_unit gpu(G, P, X, Y);
18
19    // carry_lookahead_unit (C, G, P, C0);
20    carry_lookahead_unit clu(C, G, P, Cin);
21
22    // summation_unit (S, P, C);
23    summation_unit su(S, P, C);
24
25    assign Cout = C[4];
26 endmodule // carry-lookahead_4bit
```

3. What is the gate count of your 4-bit *carry-lookahead* adder?

The gate count is 26.

4. The previous problems were concerned with a single-level 4-bit *carry-lookahead* adder. In one of the lab experiments, we will construct a 16-bit, 2-level *carry-lookahead* adder. The following questions will prepare you for this exercise. What is the propagation delay of the 16-bit, 2-level *carry-lookahead* adder in Figure 2? Likewise, what is the gate-count?

The propagation delay of the 16-bit is 6. The gate count is calculated below

$$32 + 14 \cdot 4 + 14 + 16 = 188 \text{ gates}$$